

Ken Short

© Copyright 2022 Kenneth L.
Short


1

The diagram illustrates the typical application circuit for the MCP1525, which is connected to a PIC5 MCU. The MCP1525 is a precision centration and monitoring device, and the PIC5 MCU is a microcontroller unit. The circuit includes a +5V supply, a 1 μF capacitor, and various resistors (R2, R3) and capacitors (C1, CREF+, CREF-). The PIC5 MCU is connected to the MCP1525 via its pins, and a typical waveform is shown at the bottom right, illustrating the VIn+ and VIn- signals.

© Copyright 2022 Kenneth L. Short

2

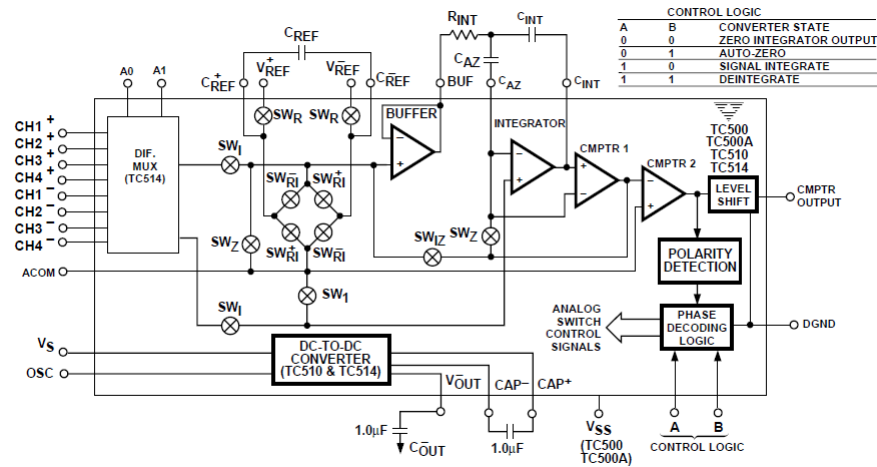Older TelCom TC514 Diagram with Correct SW_{RI} Labeling



4/18/2022

© Copyright 2022 Kenneth L. Short

3

Conversion Phases

- There are four phases that make up a single conversion of an analog input to a binary output
 - Auto Zero
 - Input Signal Integration
 - Reference Voltage Deintegration
 - Integrator Output Zero

4/18/2022

© Copyright 2022 Kenneth L. Short

4

Switch Positions vs. Conversion Phase

Conversion Phase	SW _I	SW _{R+}	SW _{R-}	SW _Z	SW _R	SW _I	SW _{Iz}
Auto-zero (A = 0, B = 1)	—	—	—	Closed	Closed	Closed	—
Input Signal Integration (A = 1, B = 0)	Closed	—	—	—	—	—	—
Reference Voltage De-integration (A = 1, B = 1)	—	*	—	—	—	Closed	—
Integrator Output Zero (A = 0, B = 0)	—	—	—	—	Closed	Closed	Closed


* Assumes a positive polarity input signal. SW_{R-} would be closed for a negative input signal.

4/18/2022

© Copyright 2022 Kenneth L.
Short

5

Typical System Timing

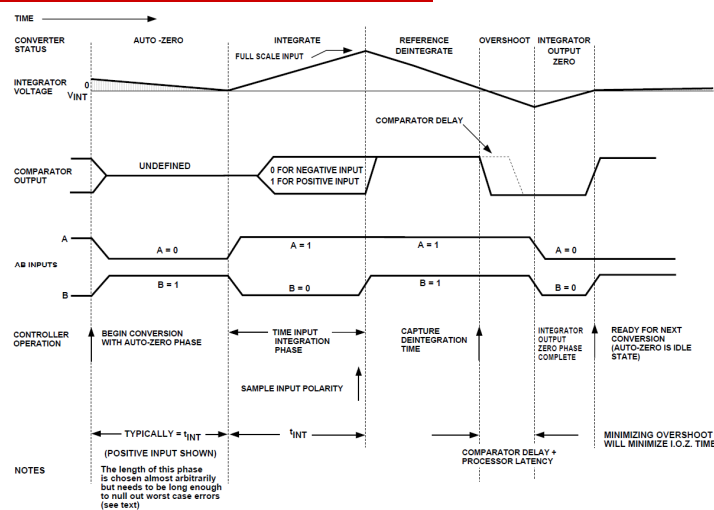


4/18/2022

© Copyright 2022 Kenneth L.
Short

6

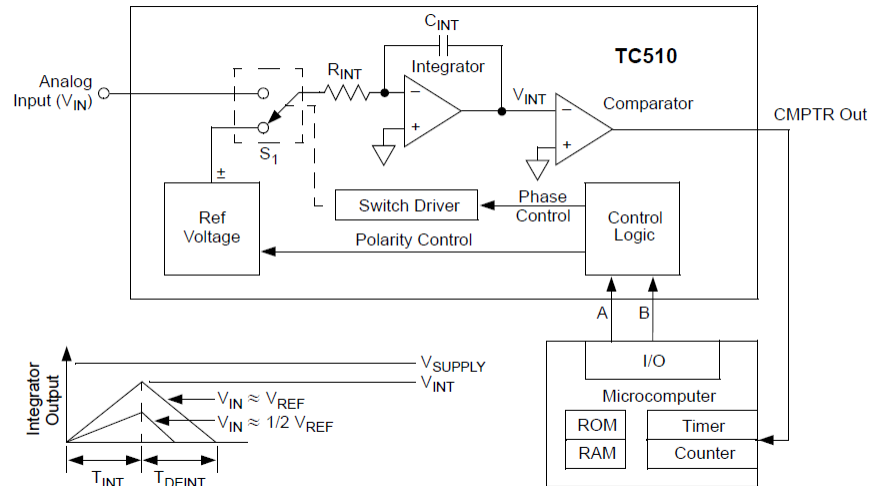Basic Dual-Slope Analog-to-Digital Converter



4/18/2022

© Copyright 2022 Kenneth L. Short

7

Relationship Between Integrate and Deintegrate Phases

$$\frac{1}{R_{INT} C_{INT}} \int_0^{t_{INT}} V_{IN}(t) dt = \frac{V_{REF} t_{DEINT}}{R_{INT} C_{INT}}$$

where:

V_{REF} = Reference Voltage

t_{INT} = Signal Integration time (fixed)

t_{DEINT} = Reference Voltage Integration time (variable)

For a constant V_{IN} :


$$V_{IN} = V_{REF} \frac{t_{DEINT}}{t_{INT}}$$

4/18/2022

© Copyright 2022 Kenneth L. Short

8

Comparator Output

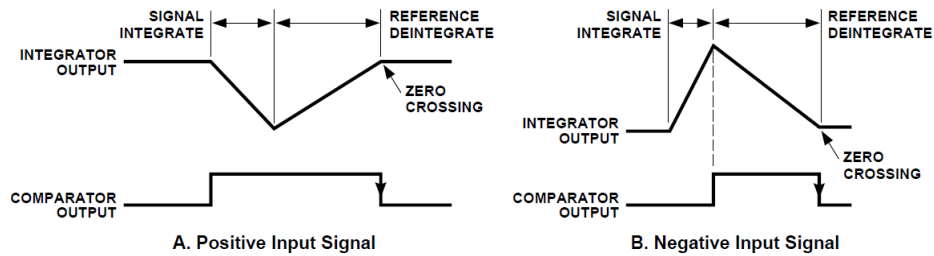


4/18/2022

© Copyright 2022 Kenneth L. Short

9

Integrator Output Zero Phase

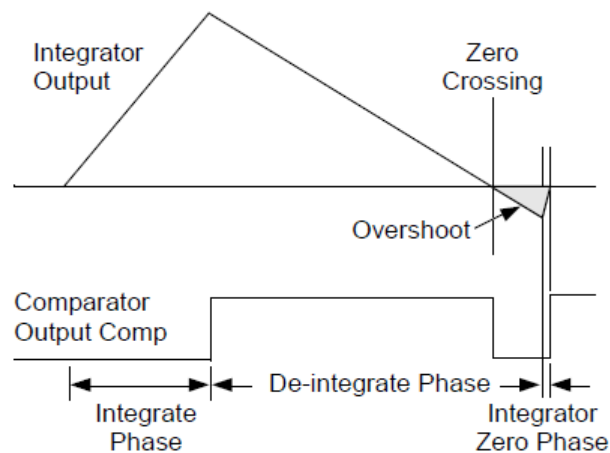

4/18/2022

© Copyright 2022 Kenneth L. Short

10

A and B Phase Control

A	B	Phase	Purpose	Duration
0	1	auto zero	correct for offset voltages	2**16 clocks minimum
1	0	signal integrate	integrate unknown input voltage	2**16 clocks exactly
1	1	reference deintegrate	integrate - Vref	until neg. edge of CMPTR
0	0	integrator zero	bring the integrator's output to 0	until pos. edge of CMPTR

4/18/2022

© Copyright 2022 Kenneth L.
Short

11

Measured Voltage vs Count


$$V_{\text{unknown}} = \frac{\text{deintegrate count}}{2^{16}} \times V_{\text{ref}}$$

4/18/2022

© Copyright 2022 Kenneth L.
Short

12

System Block Diagram

 

4/18/2022

© Copyright 2022 Kenneth L.
Short

13

Frequency Divider

```
entity freq_div is
    port (
        clk : in std_logic;           -- system clock
        rst_bar: in std_logic;        -- synchronous reset
        divisor: in std_logic_vector(3 downto 0); -- d
        clk_dvd: out std_logic);      -- output
end freq_div;
```

4/18/2022

© Copyright 2022 Kenneth L.
Short

14

Binary Counter

```
entity binary_cntr is
  generic (n : integer := 16);
  port (clk : in std_logic;           -- system clock
        cnten1 : in std_logic;       -- active high count enable
        cnten2 : in std_logic;       -- active high count enable
        up : in std_logic;           -- count direction
        clr_bar : in std_logic;      -- synchronous counter clear
        rst_bar : in std_logic;      -- synchronous reset
        q : out std_logic_vector (n-1 downto 0); -- count
        max_cnt : out std_logic);    -- maximum count indication
end binary_cntr;
```

4/18/2022

© Copyright 2022 Kenneth L.
Short

15

Out Register

```
entity out_reg is
  generic (n : integer := 16);
  port (
    clk : in std_logic;           -- system clock
    enable : in std_logic;        -- parallel load enable
    rst_bar : in std_logic;       -- synchronous reset
    d : in std_logic_vector (n-1 downto 0); -- data in
    q : out std_logic_vector (n-1 downto 0) -- data out
  );
end out_reg;
```

4/18/2022

© Copyright 2022 Kenneth L.
Short

16

TC514 Controller FSM


```
entity TC514fsm is
  port (
    soc : in std_logic;           -- start conversion control input
    cmptr : in std_logic;         -- TC 514 comparator status input
    max_cnt : in std_logic;       -- maximum count status input
    clk : in std_logic;           -- system clock
    clk_dvd : in std_logic;       -- clock divided down
    rst_bar : in std_logic;       -- synchronous reset
    a : out std_logic;            -- conversion phase control
    b : out std_logic;            -- conversion phase control
    busy_bar : out std_logic;     -- active low busy status
    cnt_en : out std_logic;       -- counter enable control to counter
    clr_cntr_bar : out std_logic; -- signal to clear counter
    load_result : out std_logic;  -- load enable
  );
end;
```

4/18/2022

© Copyright 2022 Kenneth L.
Short

17

 State Diagram Generated From Code by Code2Graphics




4/18/2022

© Copyright 2022 Kenneth L.
Short

18

TC514cntrl: Top-Level Block Diagram

 

4/18/2022

© Copyright 2022 Kenneth L.
Short

19

Use of Generics in This Design


- ❑ Appropriate entities use a generic n to specify the width of some of the design registers.
- ❑ This allows the resolution of the analog-to-digital converter to be changed in one place to change the entire design.
- ❑ Use of a small value of n is particularly useful during simulation.

4/18/2022

© Copyright 2022 Kenneth L.
Short

20

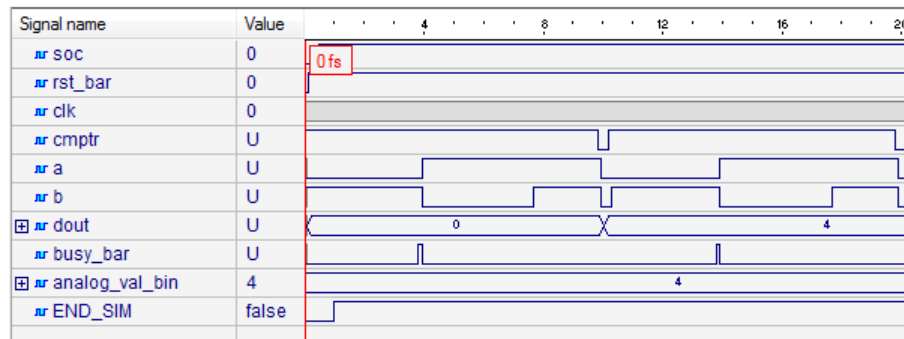Using Generic in Simulation, with $n = 4$




4/18/2022

© Copyright 2022 Kenneth L. Short

21

Looking at Internal Signals and Variables

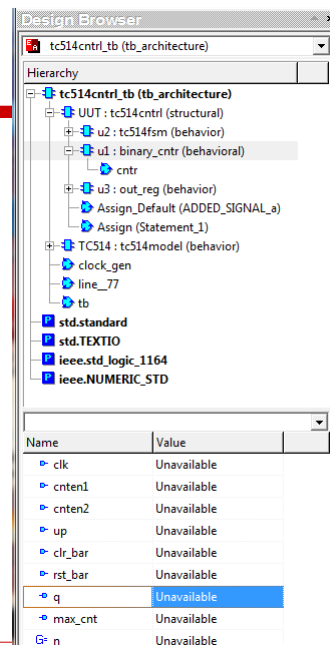- With simulation we can look at internal signals and variables in component entities




4/18/2022

© Copyright 2022 Kenneth L. Short

22

Looking at the Binary Counter's Value

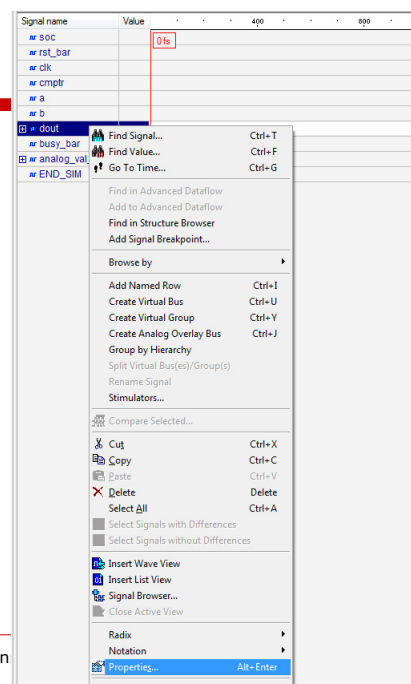- ☐ Add signal q from the tc514cntrl.
- ☐ Right click on q and select properties.




4/18/2022

© Copyright 2022 Ken Short

Displaying a Vector as an Analog Value

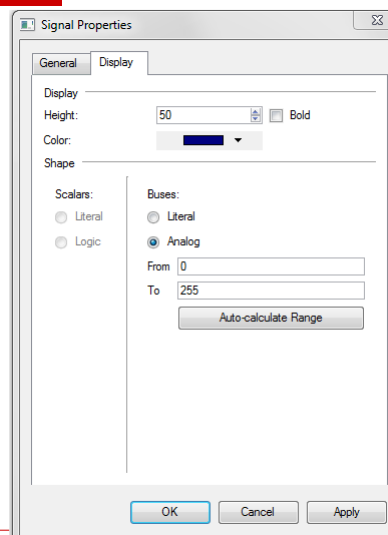- ☐ In the properties box select the Display tab.
- ☐ Set Height to 100.
- ☐ Select Analog for Buses




4/18/2022

© Copyright 2022 Kenneth L. Short

24

 q Vector Displayed as Analog Signal (n = 8)




4/18/2022

© Copyright 2022 Kenneth L. Short

25

Basics for a Self-Checking Testbench

 


4/18/2022

© Copyright 2022 Kenneth L. Short

26

Testbench's TC514 Model

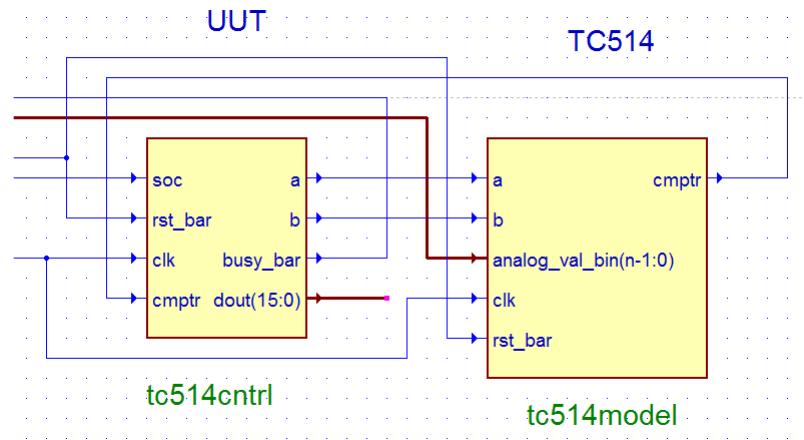


4/18/2022

© Copyright 2022 Kenneth L. Short

27

TC514 Model Diagram

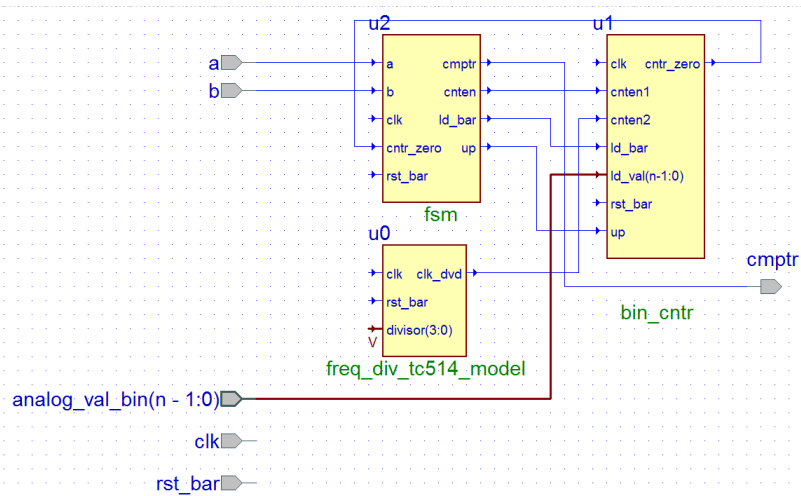


4/18/2022

© Copyright 2022 Kenneth L. Short

28

State Diagram for TC514 Model FSM

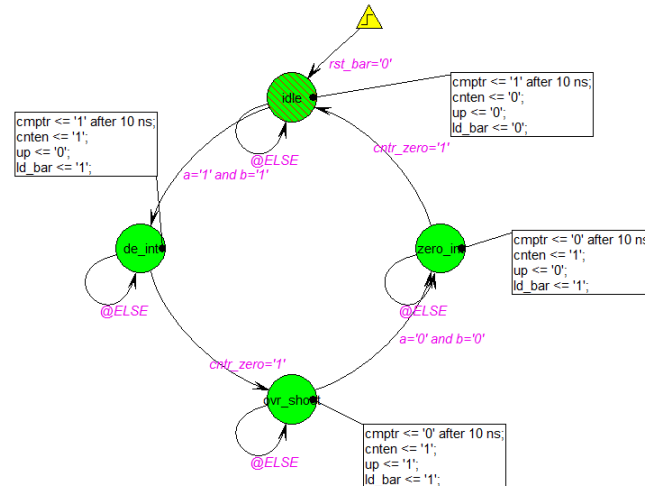

4/18/2022

© Copyright 2022 Kenneth L. Short

29

State Assignment Approaches for Moore FSMs

```

-- to automatically create state assignment the following signal declaration
-- and constant declarations must be commented out and states enumerated:

-- (load_result, clr_cntr_bar, cnt_en, busy_bar, a, b) <= present_state;

signal present_state, next_state : std_logic_vector(5 downto 0);
constant auto_zero: std_logic_vector (5 downto 0) := "011001";
constant az_idle: std_logic_vector (5 downto 0) := "000101";
constant integrate: std_logic_vector (5 downto 0) := "011010";
constant deintegrate: std_logic_vector (5 downto 0) := "011011";
constant zero_int: std_logic_vector (5 downto 0) := "110000";
constant clear_cntr: std_logic_vector (5 downto 0) := "000001";

-- to automatically create state diagram the following type declaration
-- and signal declaration must be uncommented:

-- type state is (auto_zero, az_idle, integrate, deintegrate, zero_int,
-- clear_cntr);
-- signal present_state, next_state : state;
    
```

4/18/2022

© Copyright 2022 Kenneth L. Short

30

What is the Synplify Symbolic FSM Compiler

- ❑ The Symbolic FSM Compiler is an advanced state machine optimizer, which automatically recognizes state machines in your design and optimizes them.
- ❑ Unlike other synthesis tools that treat state machines as regular logic, the FSM Compiler extracts the state machines as symbolic graphs, and then optimizes them by re-encoding the state representations and generating a better logic optimization starting point for the state machines.
- ❑ The FSM Explorer uses the state machines extracted by the FSM Compiler when it explores different encoding styles.
- ❑ The FSM Explorer option is only available in the Synplify Pro and Synplify Premier tools.

4/18/2022

© Copyright 2022 Kenneth L.
Short

31

State Assignment


- ❑ If your design does not specify state assignment, the Synplifier synthesizer contains a feature called FSM Compiler that identifies FSMs in your description and optimizes their state assignments based on the target PLD
- ❑ If you specified state assignment in your FSM description, make sure Synplify's FSM Compiler is OFF when you run the synthesis.

4/18/2022

© Copyright 2022 Kenneth L.
Short

32

Turning OFF FSM Compiler

 

4/18/2022

© Copyright 2022 Kenneth L.
Short

33